
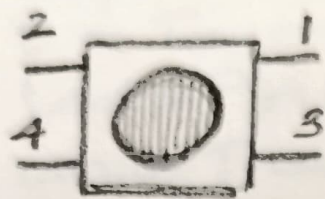


* PUSH BUTTON


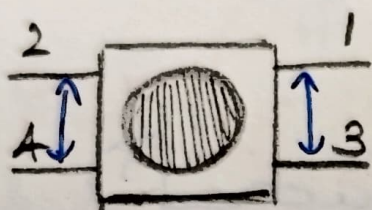


(1,2) → Internally Connected
(3,4) → Internally Connected

When pushed




(1,3) are Connected
(2,4) are Connected

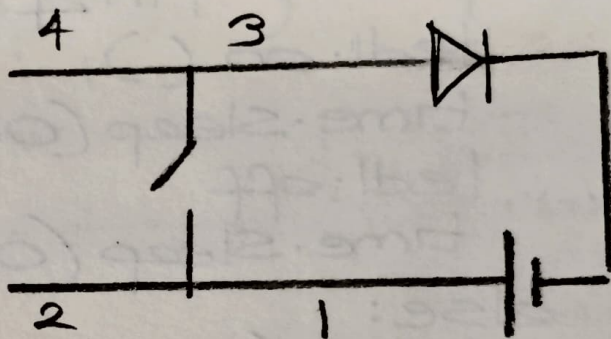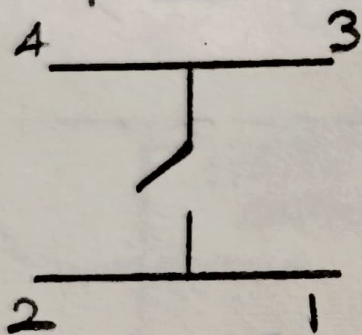


PULL UP RESISTOR

Internal resistor that pulls up GPIO to a specific resistance

Before pushing

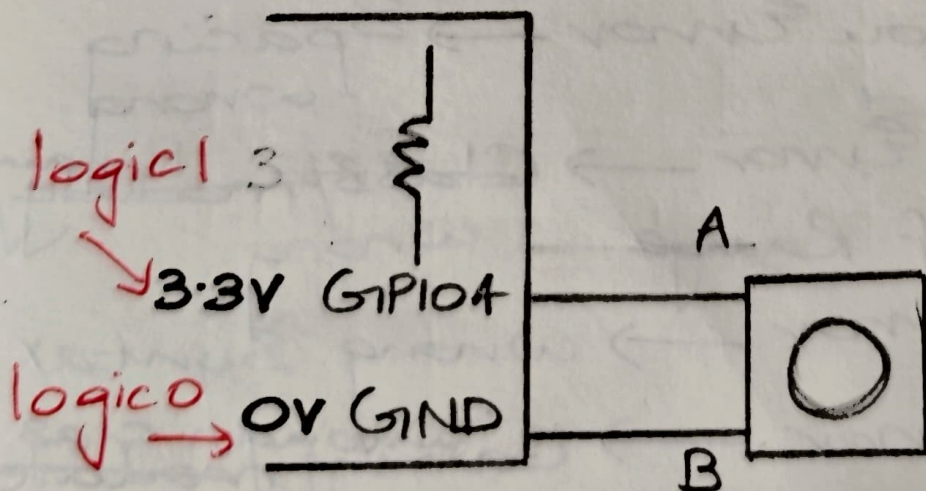

After pushing ✓

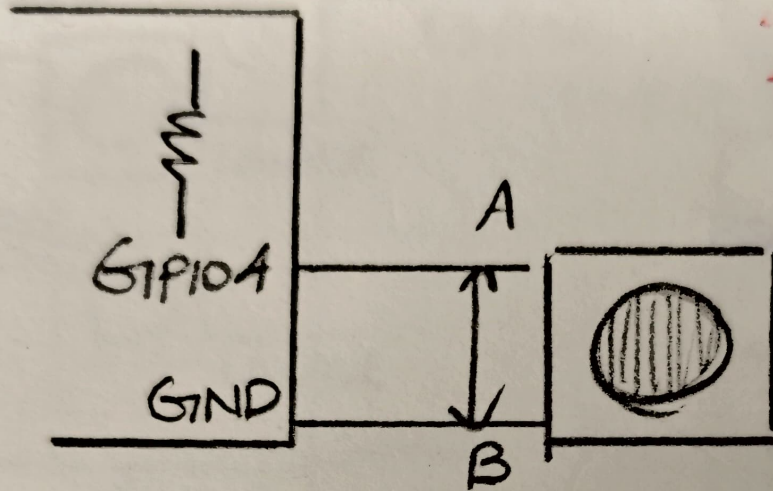

A & B are connected

$\therefore \text{GPIO4} = \text{GND}$

$\Rightarrow \text{GPIO4} = 0\text{V}$