
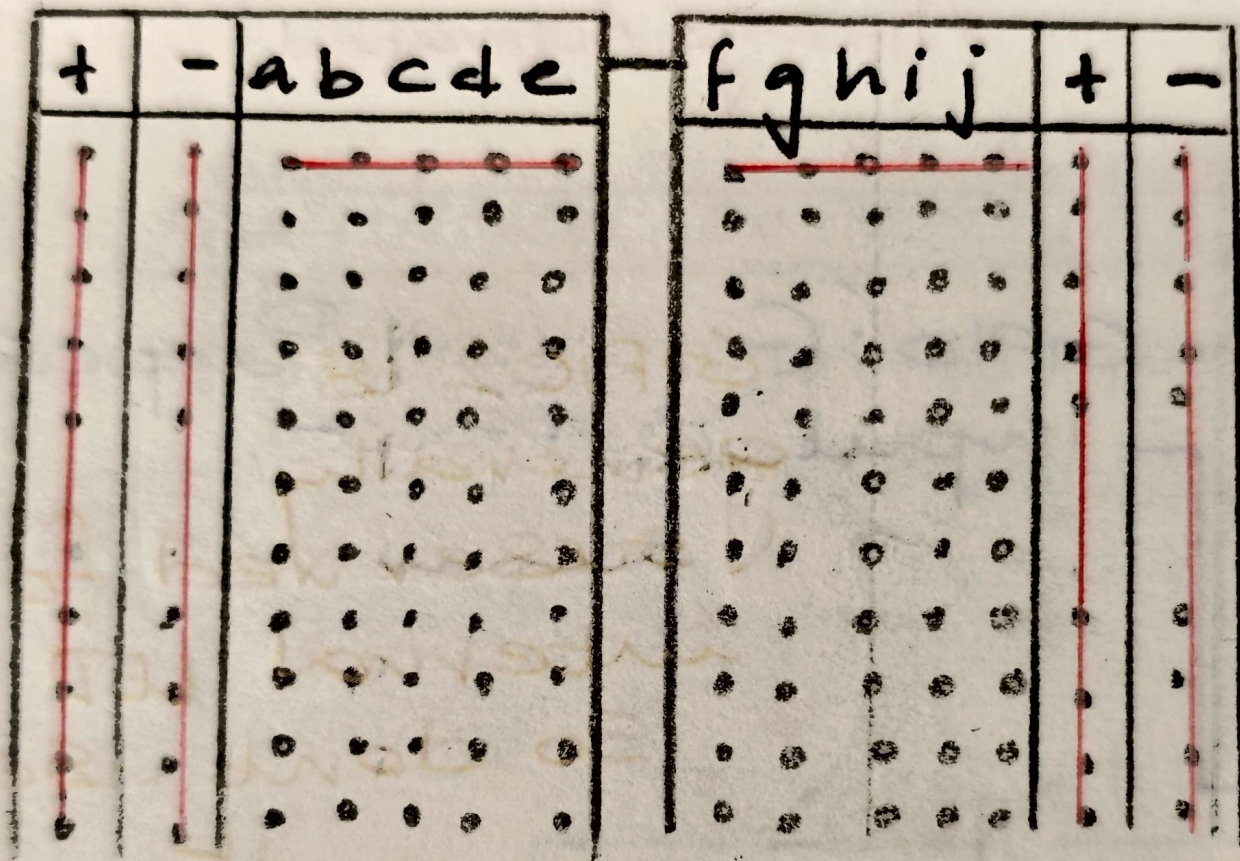


* BREADBOARD

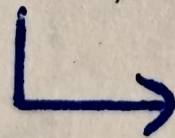


Connected
vertically




Connected
horizontally
(abcde / fg hij)

* LIMIT SWITCH

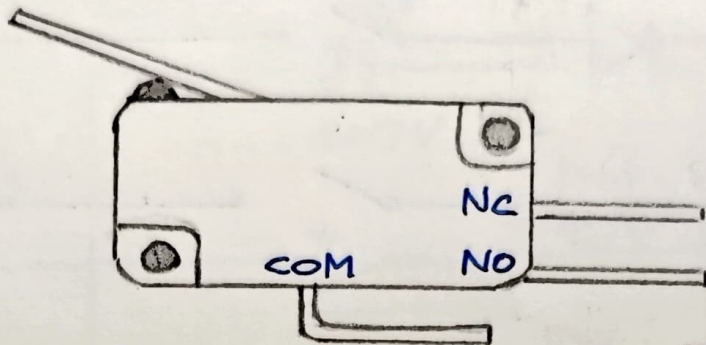


{ COM → Common Terminal
NC → Normally Closed
NO → Normally Open }

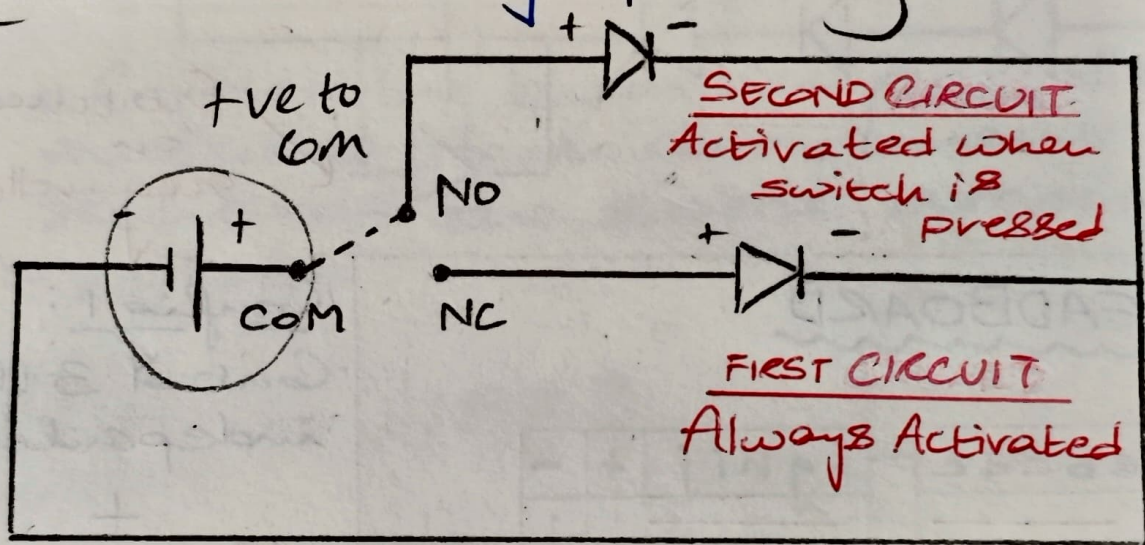


* ESP32

GPIO: General Purpose Input Output

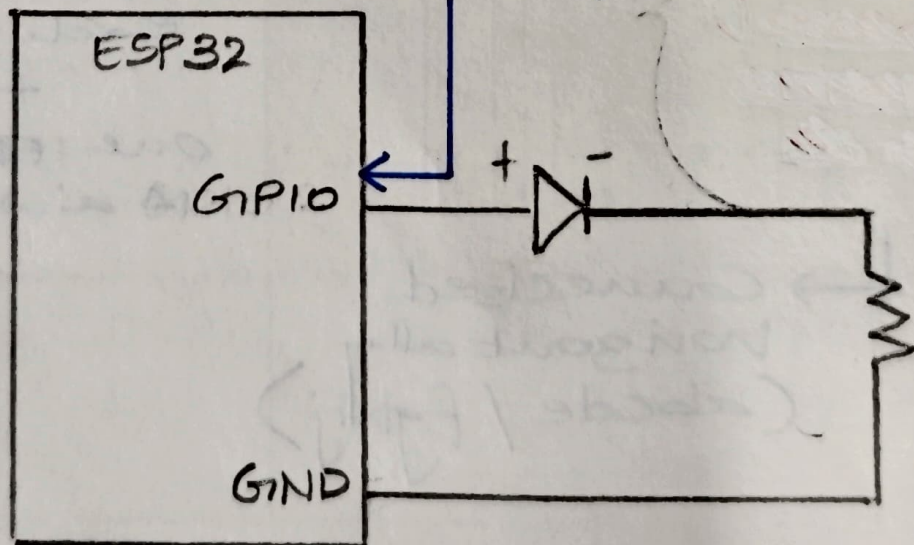

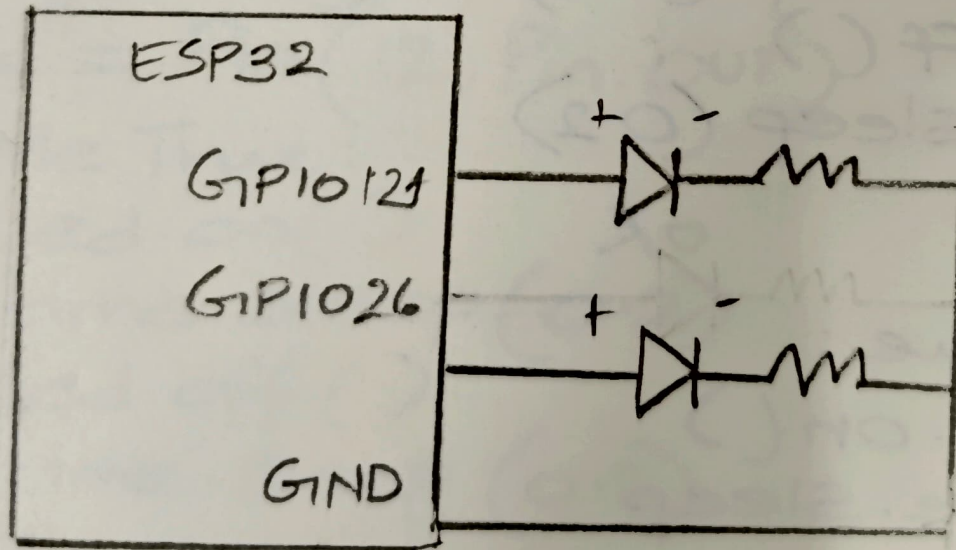- GPIO2 → Reserved for internal LED
- Openport → floating condition (port not connected to anything)
- Resistors are connected to manage the flow of current from ESP32 to prevent damage to the components
 - -ve to GND



Two ext LEDs are in || as voltage is insufficient in series